
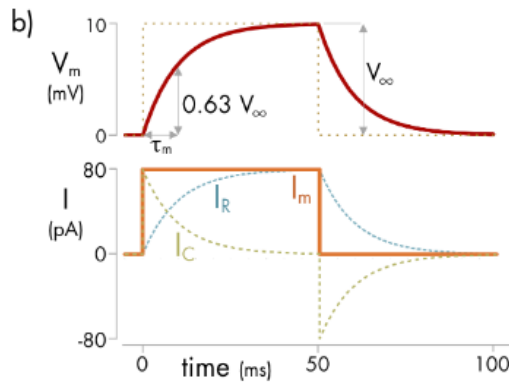


Spiking Neural Nets:

Latency coding:

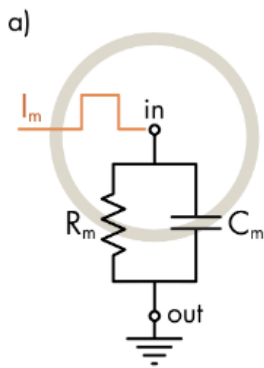

— basic neurons
can be represented
as RC circuits

— resistor controls
discharge and charge
rate of capacitor

R_m = conductance of cell membrane

C_m = capacitance of entire membrane

RC time constant = τ = time (sec) it takes to discharge
63.3%

What is shown in the voltage graph is the response of C_m as a square wave current is injected. This is the behaviour of an integrator parallel RC circuit.

The expected voltage response if there was only a resistor in the circuit is shown as the dashed line.

→ capacitor slows voltage response

$$V_m \rightarrow 10V \begin{cases} I_C \rightarrow 0 \\ I_R \rightarrow I_m \end{cases} \text{ where } I_m = I_C + I_R$$

- When current is injected, it either flows through C_m or R_m
- current flow into C_m is proportional to the ROC at the membrane potential
 - at first the ROC is fast and all the injected current flows into the capacitor
 - as charge flows into the capacitor the voltage across the circuit increases in proportion to the amount of charge transferred

$$V_m = \frac{q}{C_m}$$

increase in V_m results in an increasing fraction of the current flowing through the resistor and ROC of V_m declines

$$I_R = V_m / R_m \quad I_C = C_m \frac{dV_m}{dt}$$

Combining and rearranging gives a differential equation

For the dynamic change in voltage in response to current injection.

$$I_m = \frac{V_m}{R_m} + C_m \frac{dV_m}{dt}$$

$$I_m - \frac{V_m}{R_m} = C_m \frac{dV_m}{dt}$$

$$\frac{R_m I_m - V_m}{R_m C_m} = \frac{dV_m}{dt}$$

$$\tau_m \frac{dV_m(t)}{dt} = -V_m(t) + R_m I_m(t)$$

$$\tau_m = R_m C_m \rightarrow \text{time constant}$$

↗ determines rate of change of the voltage

if current is injected at $t = 0$, change in voltage defined as:

$$V_m(t) = V_{\infty} (1 - e^{-t/\tau_m})$$

max voltage ↗

larger τ_m = slower ROC of V_m

Similarly, change in voltage at the offset is given by:

$$V_m(t) = V_{\infty} e^{-t/\tau_m} \} \text{ simple exponential decay}$$

